

EXPERIMENT-1

Name:- Julakanti Sravani

Roll No:- 241210052

Branch:- CSE-1

Subject:- Computer Architecture and Organization

Subject code:- CSBB 251


Aim:- To build and simulate circuits of - 8x1 Multiplexer using multiplexer and 2x1 multiplexers, 8x3 encoder using priority encoder and OR gates

Software tools used:-


Logisim

Procedure:-

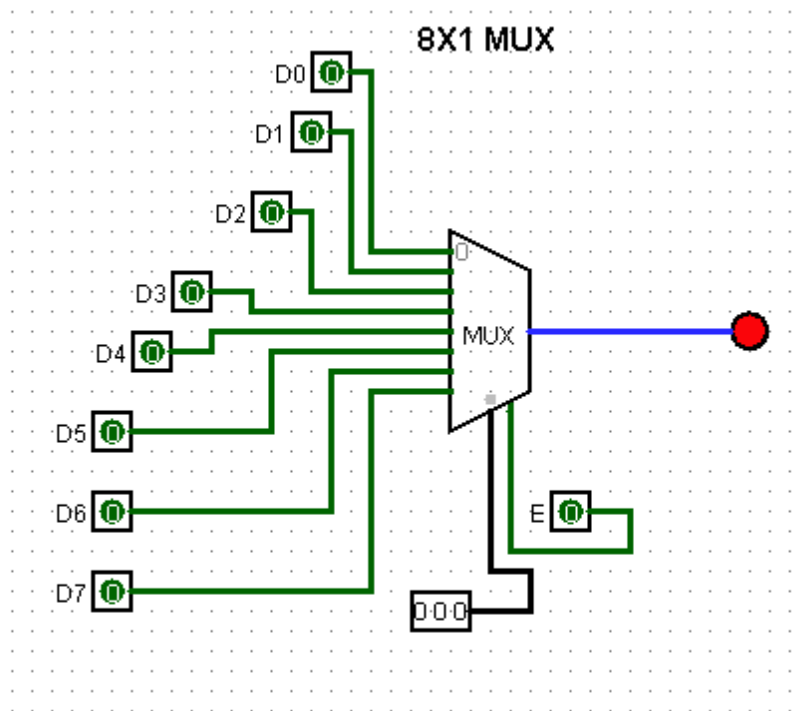
1. Build the following circuits using required components in logisim.
2. Verify the working of circuits using truth tables.



8X1 MUX USING 2X1 MUX

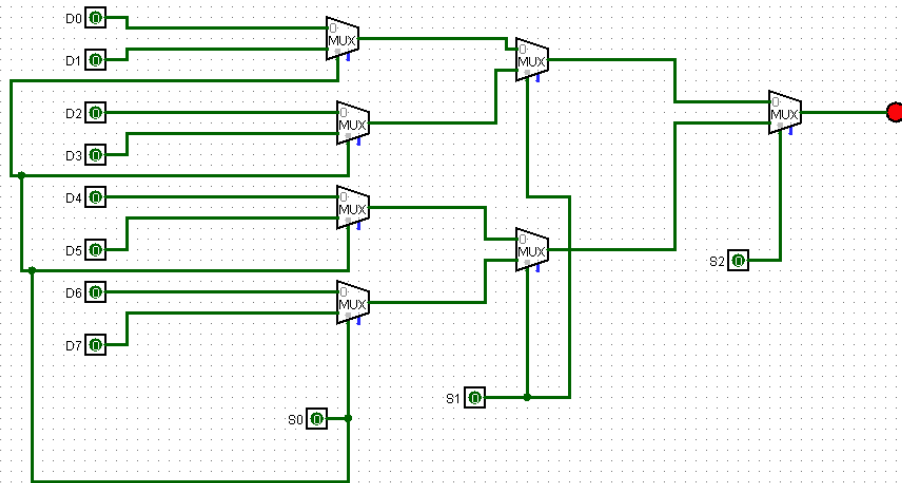

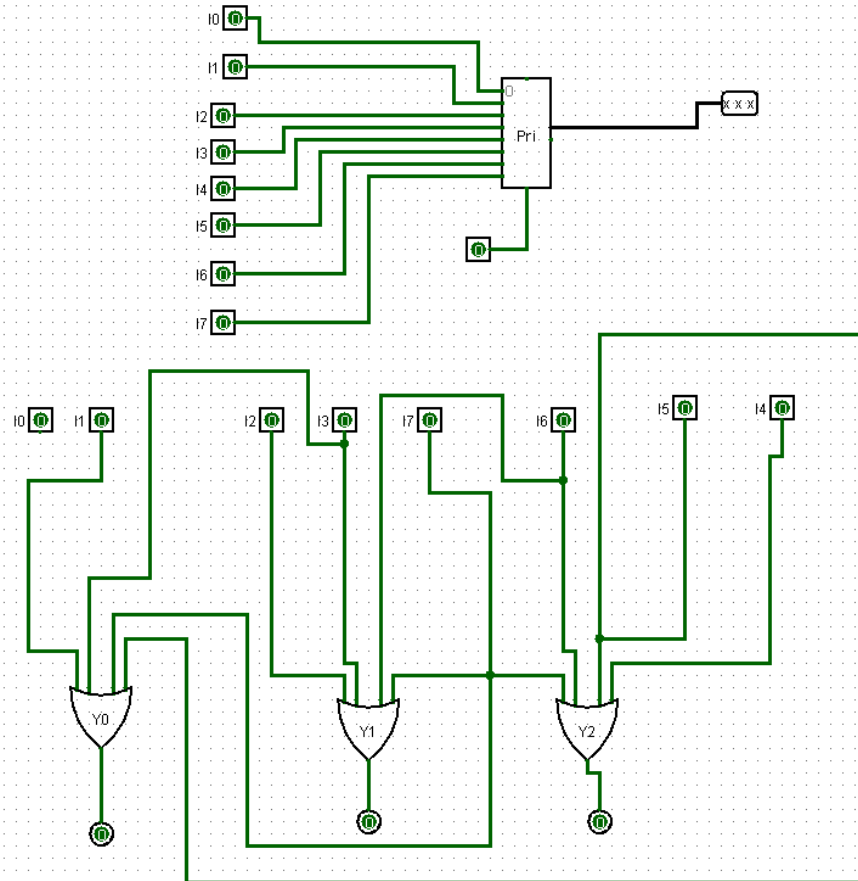8X3 ENCODER USING PRIORITY ENCODER AND OR GATES



Conclusion :-

Hence we successfully designed and simulated circuits of - 8x1 Multiplexer using multiplexer and 2x1 multiplexers, 8x3 encoder using priority encoder and OR gates